
Fall 2016

The required mini-project is to design and document a variable speed fan controller using a thermistor, an instrumentation amplifier and a microcontroller. The speed of the fan should gradually increase as the temperature measured by your thermistor increases. A single 5V supply will be used to power your mini-project and the fan. To ensure that the fan spins up at power on, you should provide a burst period where you run the fan at full speed for a second or two. When the temperature reaches between 80°-90°F the fan should start to increase in speed and must reach full speed between 120-130°F (PWM = 100% duty cycle). The actual RPM of the fan can be monitored through the open-collector "TACH" port on the test fixture where the speed is represented a 2 ticks per rotation.

## **Specific Requirements:**

- 1) Demonstration of a variable speed fan controller meeting the following specs:
  - a. At power up the controller will burst the fan then hold at an idle speed.
  - b. The fan will transition to first speed above idle between 80°- 90°F.
  - c. The fan will spin at full speed between 120°-130° and above.
  - d. There must be at least 12 different fan speeds between 80° and 130°F.
  - e. The amplifier, microcontroller and fan run from the same 5V supply.
- 2) Submission of a detailed schematic of your actual circuit. The schematic can be created in a CAD package like Mentor Graphics Design Capture or may be neatly hand drawn.
- 3) Submission of cleanly formatted source code of your actual design.
- 4) Submission of a one page, typed, single spaced report describing the functionality of the hardware and software of your variable speed fan controller design.
- 5) Be able to describe the circuit design and software operation of your system.

## **Mini-Project Test Fixture:**

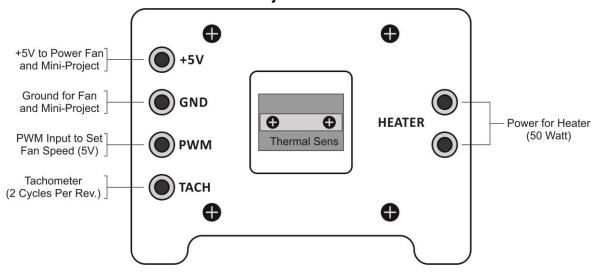

- \* The Grade for Mini-Projects submitted after 28 October will be reduced by 10% per class day.
- \*\* Failure to complete the Mini-Project will result in a grade of "Incomplete" for the class.