

Name \_\_\_\_\_


Lab Section \_\_\_\_\_

## Sensors and Sensor Interfacing - Lab 1

### Measuring Temperature with a Thermistor


The thermistor is a common electrical component used for measuring temperature. A thermistor is essentially just a temperature sensitive resistor. Most thermistors have a negative temperature coefficient (NTC), meaning the resistance of the thermistor decreases as temperature rises. One problem often encountered when using thermistors for measuring temperature is that their temperature/resistance curve is not linear (as shown in the graph below).

| Resistance Versus Temperature |                     |
|-------------------------------|---------------------|
| Temperature C                 | Resistance $\Omega$ |
| 0                             | 94980               |
| 5                             | 74440               |
| 10                            | 58750               |
| 15                            | 46670               |
| 20                            | 37300               |
| 25                            | 30000               |
| 30                            | 24270               |
| 35                            | 19740               |
| 40                            | 16150               |
| 45                            | 13280               |
| 50                            | 10970               |
| 55                            | 9109                |
| 60                            | 7599                |
| 65                            | 6367                |
| 70                            | 5359                |
| 75                            | 4529                |
| 80                            | 3843                |
| 85                            | 3273                |
| 90                            | 2799                |
| 95                            | 2402                |
| 100                           | 2069                |

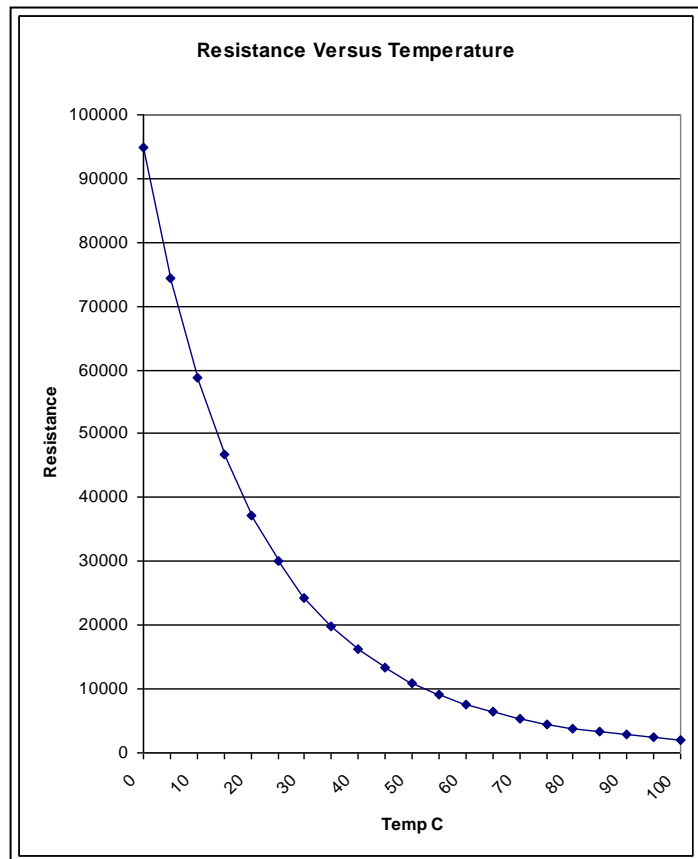

The non-linearity of the thermistor is generally not a problem when it is integrated into a digital system where a look-up table can be used to properly convert the measurements.

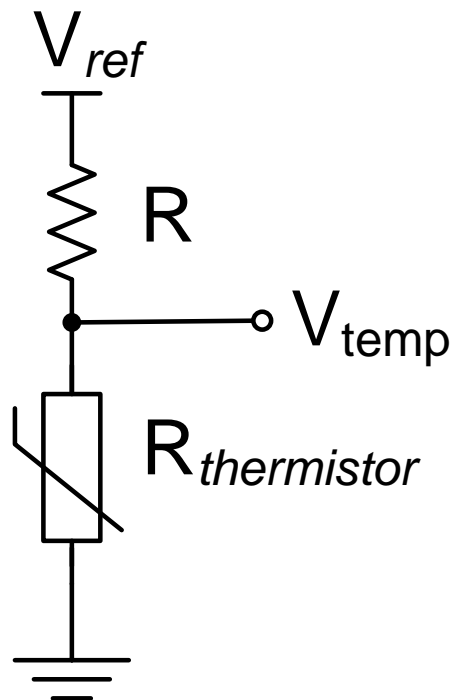A simple way to convert a changing temperature into a changing voltage with a thermistor is to place it in series with a fixed value resistor creating a voltage divider. By placing a stable DC voltage across the pair, the varying thermistor resistance will result in a varying DC voltage at the junction of the two parts.




The voltage at the node  $V_{temp}$  represents current temperature as determined by the following voltage divider equation:

$$V_{temp} = V_{ref} \left( \frac{R_{Thermistor}}{R + R_{Thermistor}} \right)$$
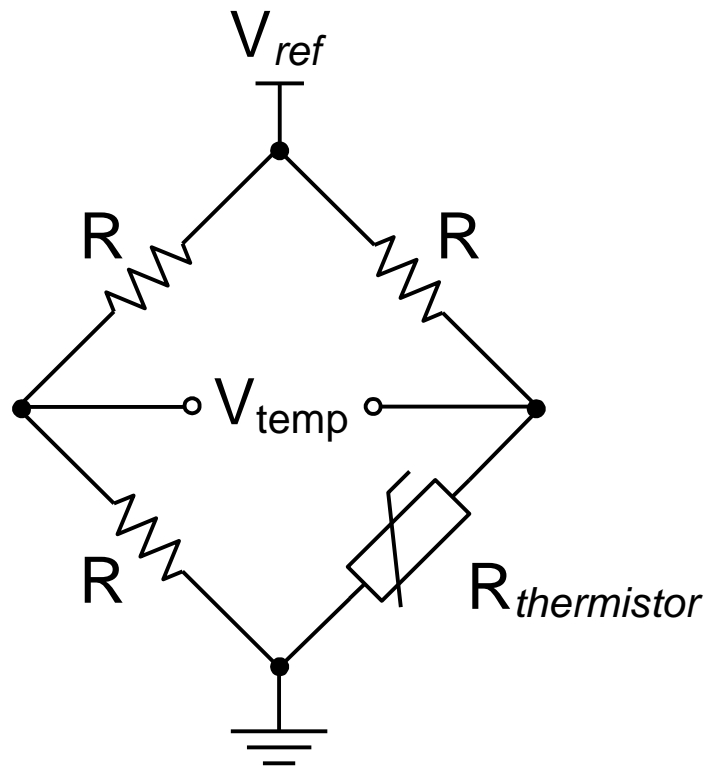
### Wheatstone bridge:

Sometimes, the simple ground referenced voltage divider will not meet the performance requirements needed when converting a resistance to a voltage. A more precise method for converting a resistance in to a voltage can be achieved by using a Wheatstone bridge topology.




The output of the single element varying Wheatstone bridge can be computed with the following equation:


$$V_{temp} = V_{ref} \left( \frac{1}{2} - \frac{R_{Thermistor}}{R + R_{Thermistor}} \right)$$

*Preparing the thermistor for the Lab:*

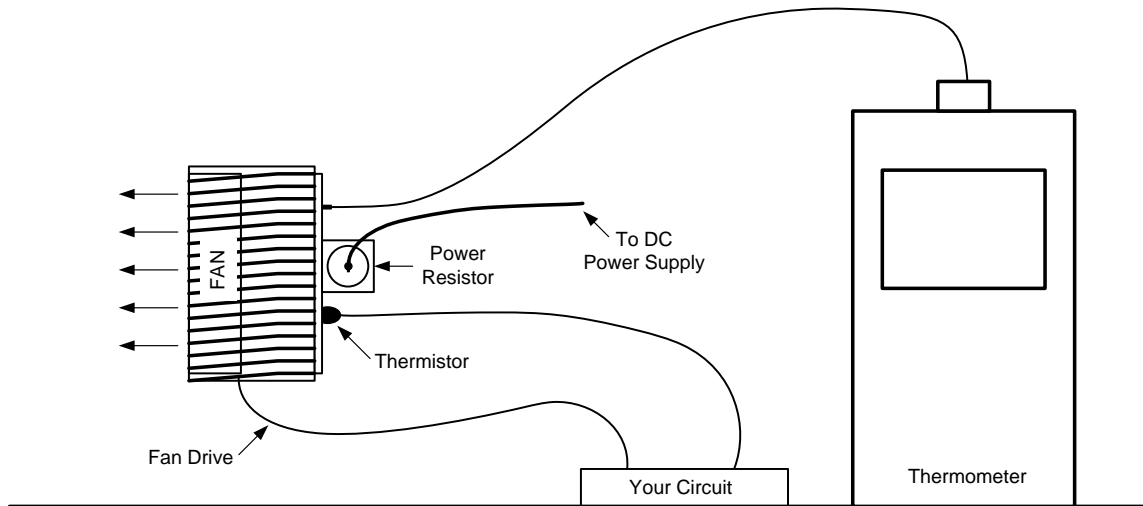In the following experiments the thermistor will be mounted to the heat sink away from the rest of the electrical circuits. To make this possible you will need to add a length of wire to the thermistor.



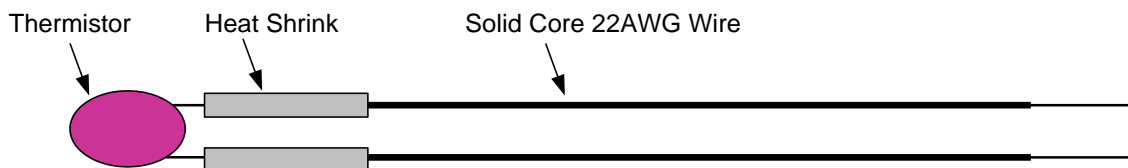Use the long green 22 AWG solid core wire from the Jameco Wire Jumper Kits in the lab. Straighten the leads on both ends of the jumper wire. Solder a wire to each lead of the thermistor. To insulate the connection cover the solder joint with heat shrink tubing.




A demonstration will be given in the lab.

*Making Measurements:*

Now you will measure the resistance of the thermistor as a function of temperature. Use the Fluke 50s digital thermometer to make the temperature measurements. The first measurement will be at room temperature which is approximately 72° F. Take resistance measurements as a function of temperature by applying heat to your thermistor. Align the digital thermometer's thermal couple close to the thermistor for best results. Use the heat source provided in the lab to raise the temperature of the thermistor and take resistance measurements to complete the table below.

| Thermistor Temperature vs. Resistance |            |
|---------------------------------------|------------|
| Temperature                           | Resistance |
| Room Temp. _____ ° F                  | _____ Ω    |
| 80° F                                 | _____ Ω    |
| 85° F                                 | _____ Ω    |
| 90° F                                 | _____ Ω    |
| 95° F                                 | _____ Ω    |
| 100° F                                | _____ Ω    |
| 105° F                                | _____ Ω    |
| 110° F                                | _____ Ω    |
| 115° F                                | _____ Ω    |
| 120° F                                | _____ Ω    |
| 125° F                                | _____ Ω    |
| 130° F                                | _____ Ω    |

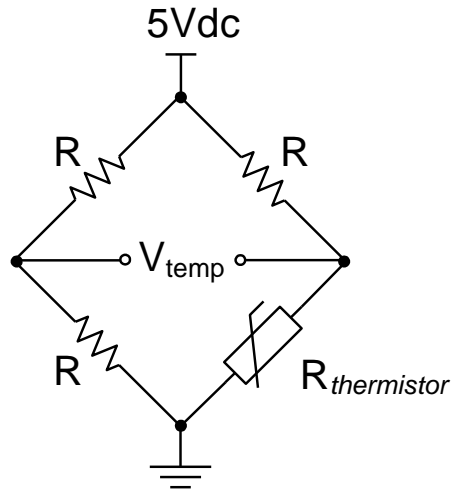Now build a circuit using the thermistor in a Wheatstone bridge topology. Use resistor values for the Wheatstone bridge that are approximately twice the "room temperature" value of your thermistor. Make sure the three resistors are matched in value within 1%. Use a  $V_{ref}$  of 5Vdc to power your circuit. Complete the table below:



| Thermistor Temperature vs. Voltage |          |
|------------------------------------|----------|
| Temperature                        | Voltage  |
| Room Temp. _____ ° F               | _____ mV |
| 80° F                              | _____ mV |
| 85° F                              | _____ mV |
| 90° F                              | _____ mV |
| 95° F                              | _____ mV |
| 100° F                             | _____ mV |
| 105° F                             | _____ mV |
| 110° F                             | _____ mV |
| 115° F                             | _____ mV |
| 120° F                             | _____ mV |
| 125° F                             | _____ mV |
| 130° F                             | _____ mV |