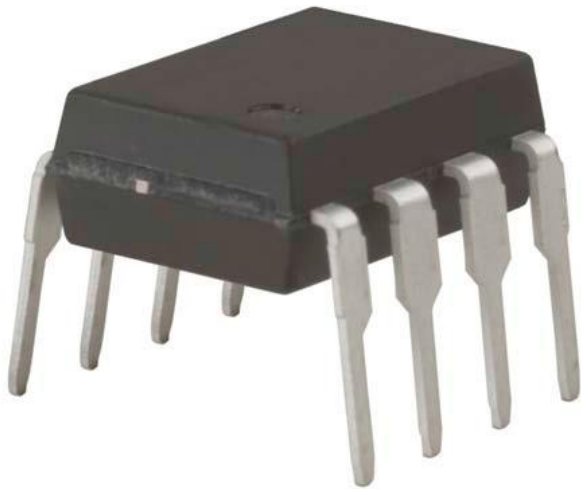


Op Amps & Instrumentation Circuits




ECE Senior Design
7 February 18

Ideal Op Amp Characteristics

- Infinite Voltage Gain $A_{vo} = \infty$
- Infinite Input Resistance $r_{in} = \infty$
- Zero Output Resistance $r_o = 0$
- Infinite Bandwidth $BW = \infty$
- Zero Input Offset Voltage $V_o = 0$ if $V_{in} = 0$


Op Amp Symbol

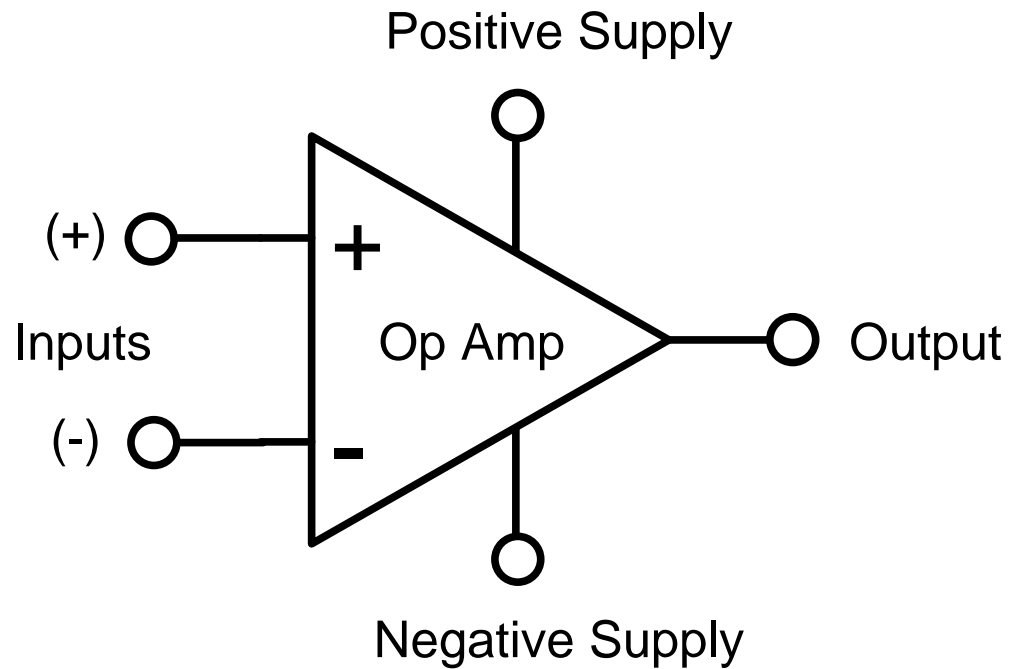

Op Amp Topologies


- Inverting Amplifiers
- Non-Inverting Amplifiers
- Differential Amplifiers

Inverting Op Amp

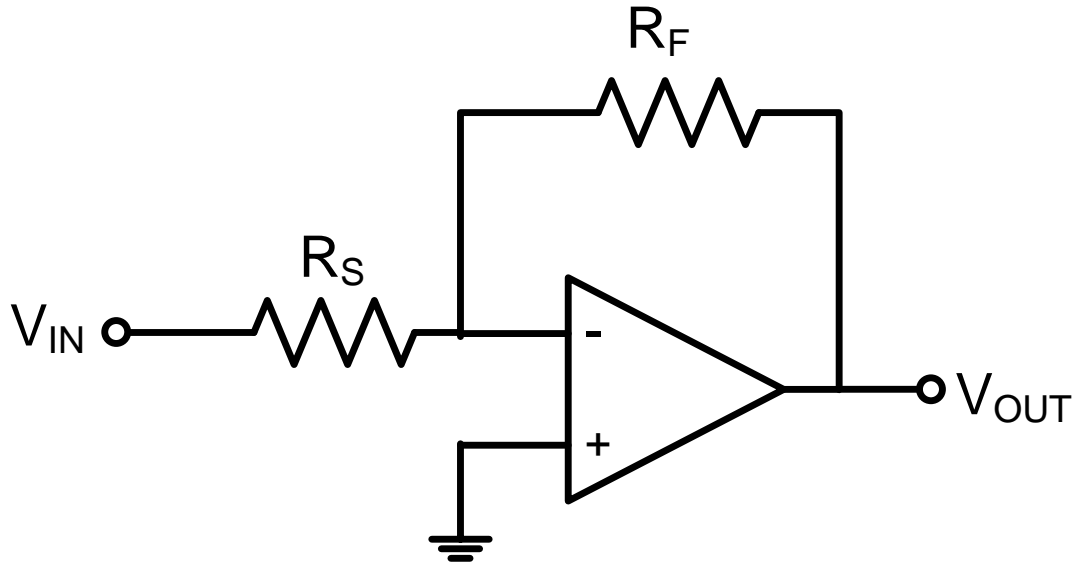


$$\frac{V_{OUT}}{V_{IN}} = \frac{-R_F}{R_S}$$

Inverting Op Amp Single Supply

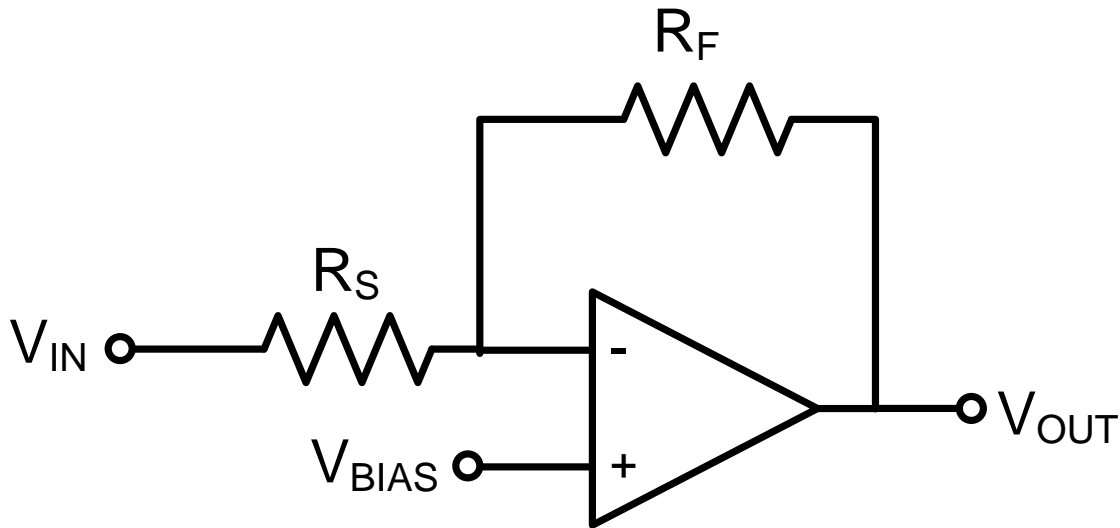


$$\frac{V_{OUT} - V_{BIAS}}{V_{IN} - V_{BIAS}} = \frac{-R_F}{R_S}$$

Non-Inverting Op Amp

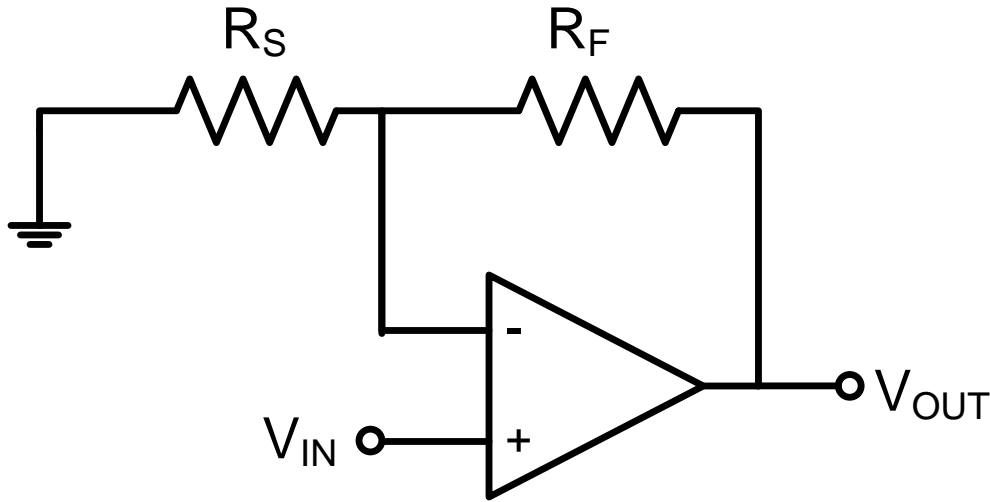


$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_F}{R_S}$$

Non-Inverting Op Amp Single Supply

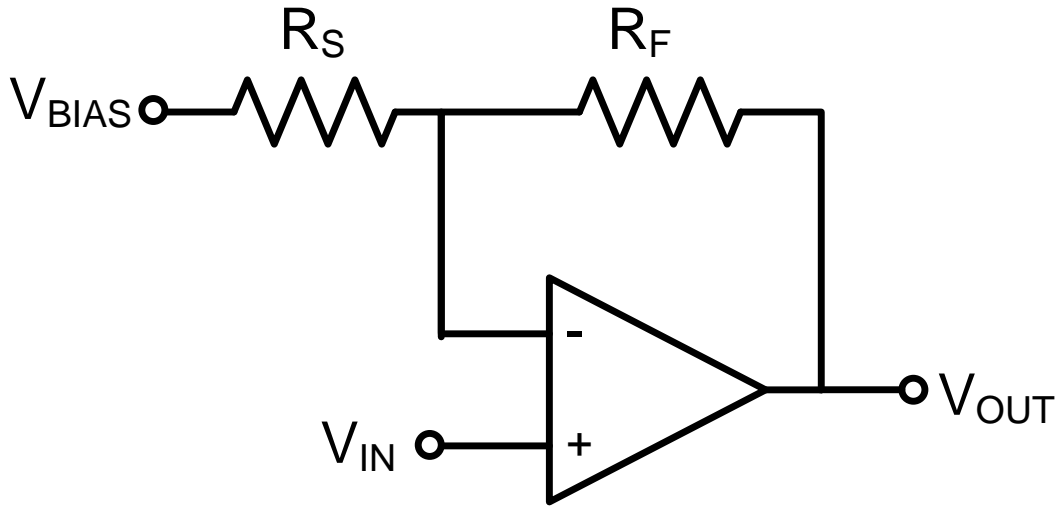


$$V_{OUT} = V_{IN} + \frac{(V_{IN} - V_{BIAS})R_F}{R_S}$$

Difference Amplifier

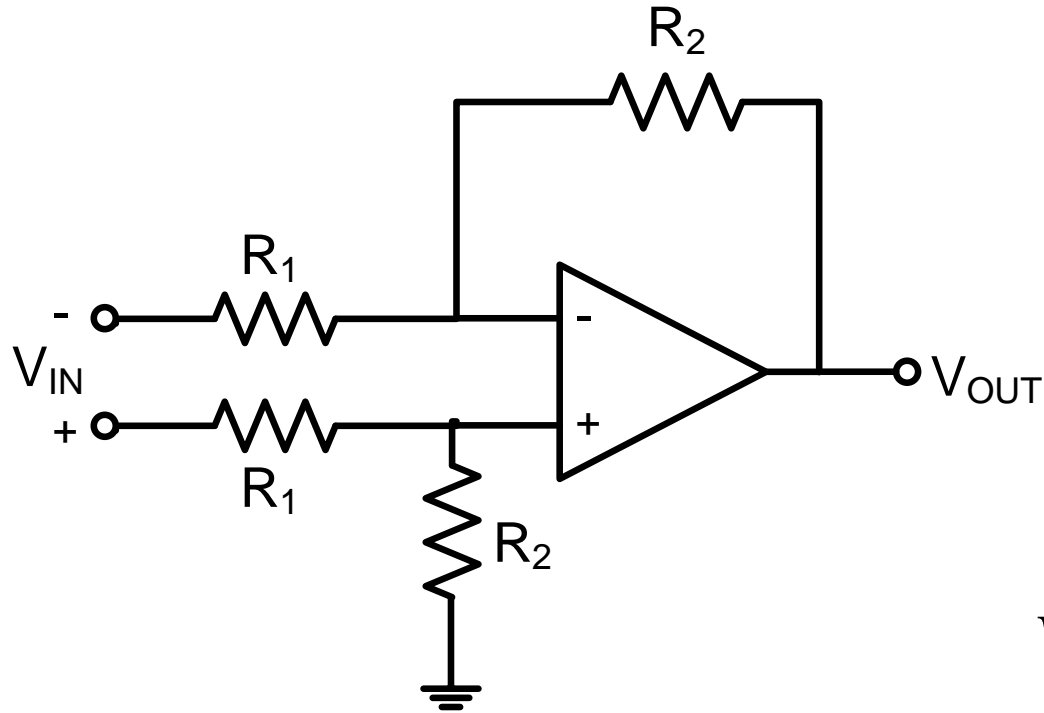


$$\frac{V_{OUT}}{V_{IN}} = \frac{R_2}{R_1}$$

Op Amps in Active Filters

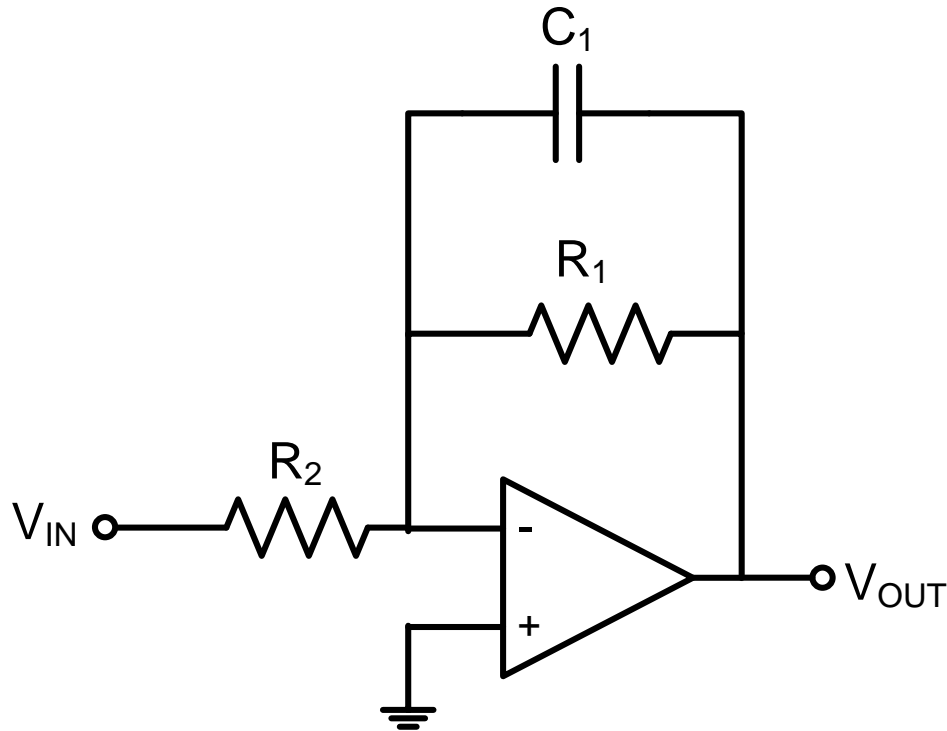


$$f_c = \frac{1}{2\pi(R_1 C_1)}$$

Adjusting Gain

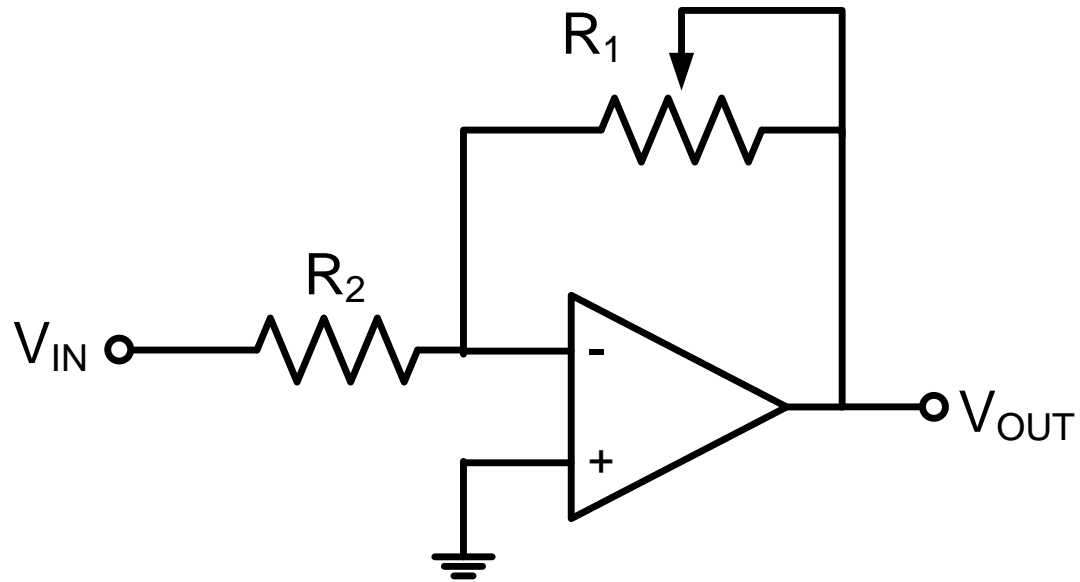

Op Amp as a Comparator

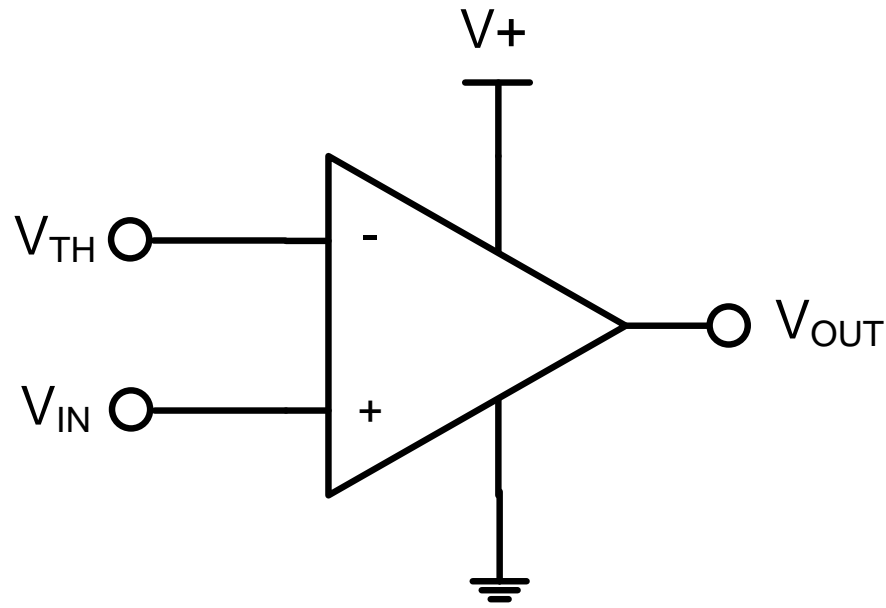


IF ($V_{IN} > V_{TH}$)
Then $V_{OUT} = V+$


Else

$V_{OUT} = GND$


Power Supply Decoupling

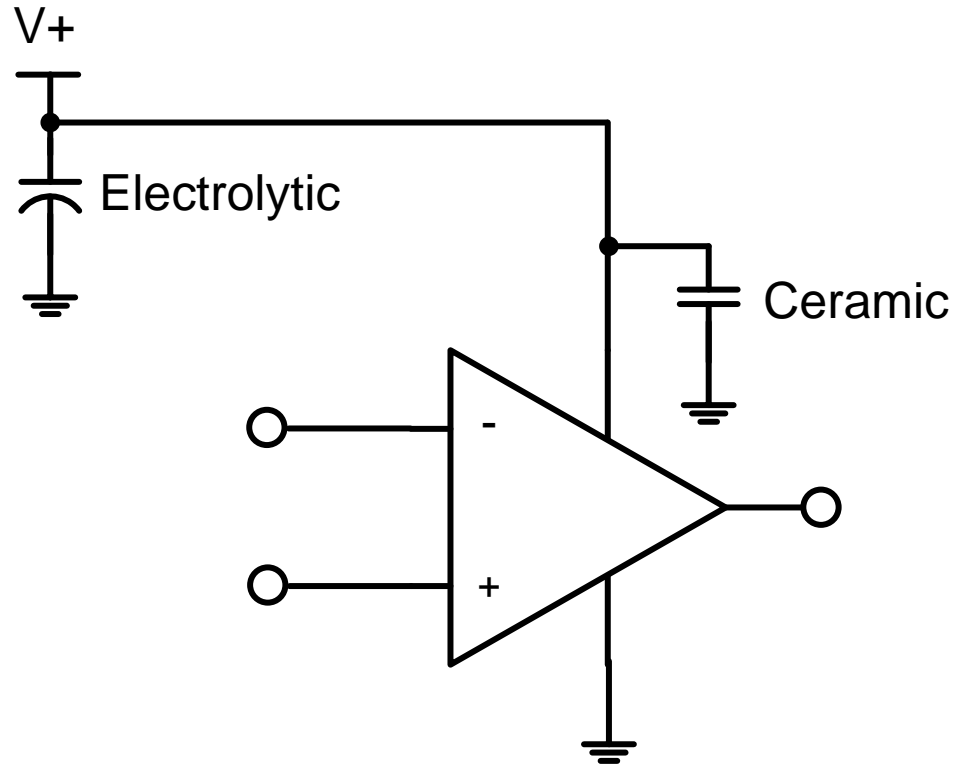


Common Op Amp Packages

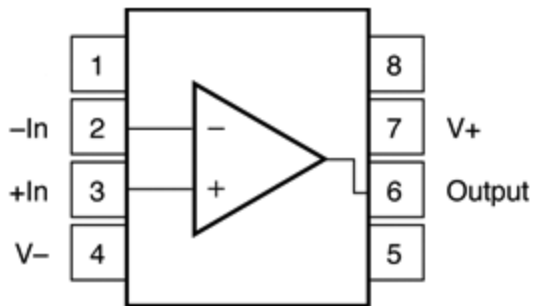




Single

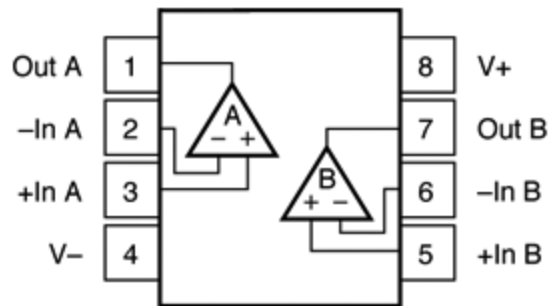


Dual

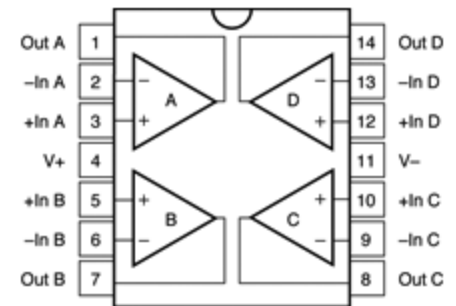

Quad

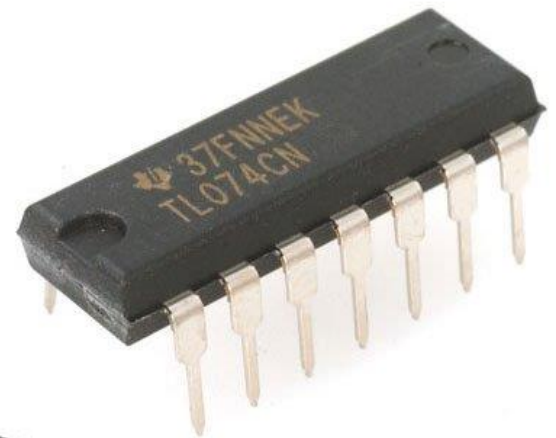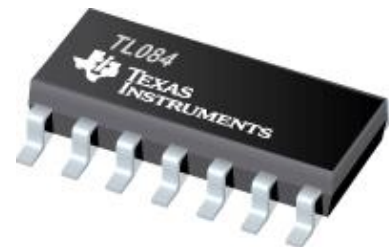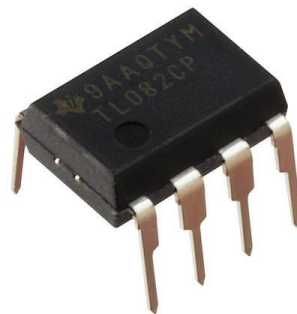


Terminating Unused Op Amps

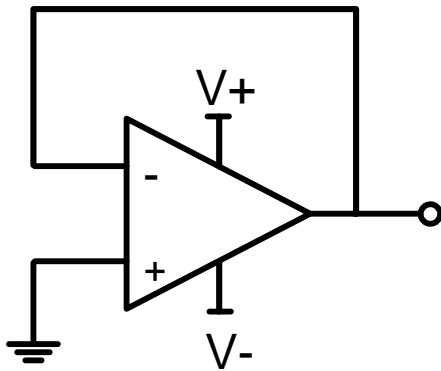


Bi-Polar Supply

- Close Loop
- Gnd + Input

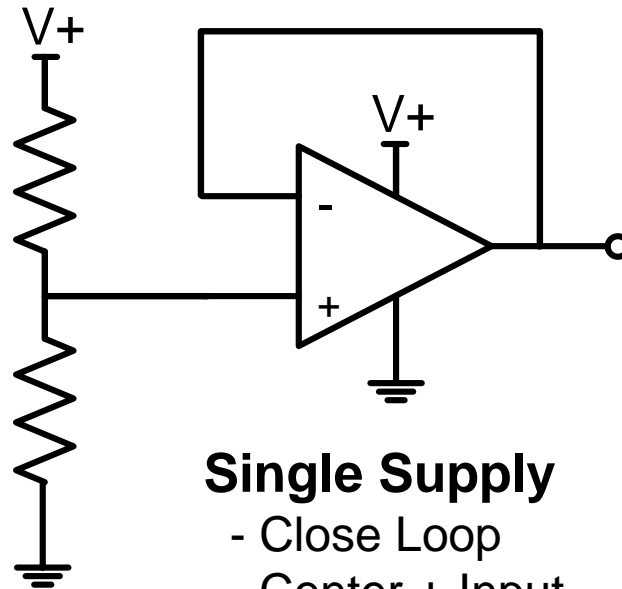

Single Supply


- Close Loop
- Center + Input

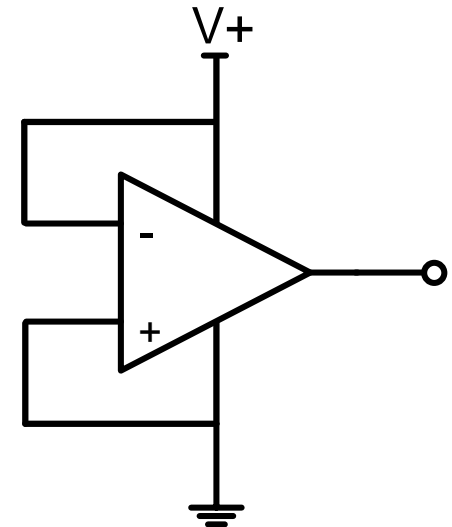


Comparator

- Tie Inputs to Rails


Instrumentation Amplifiers

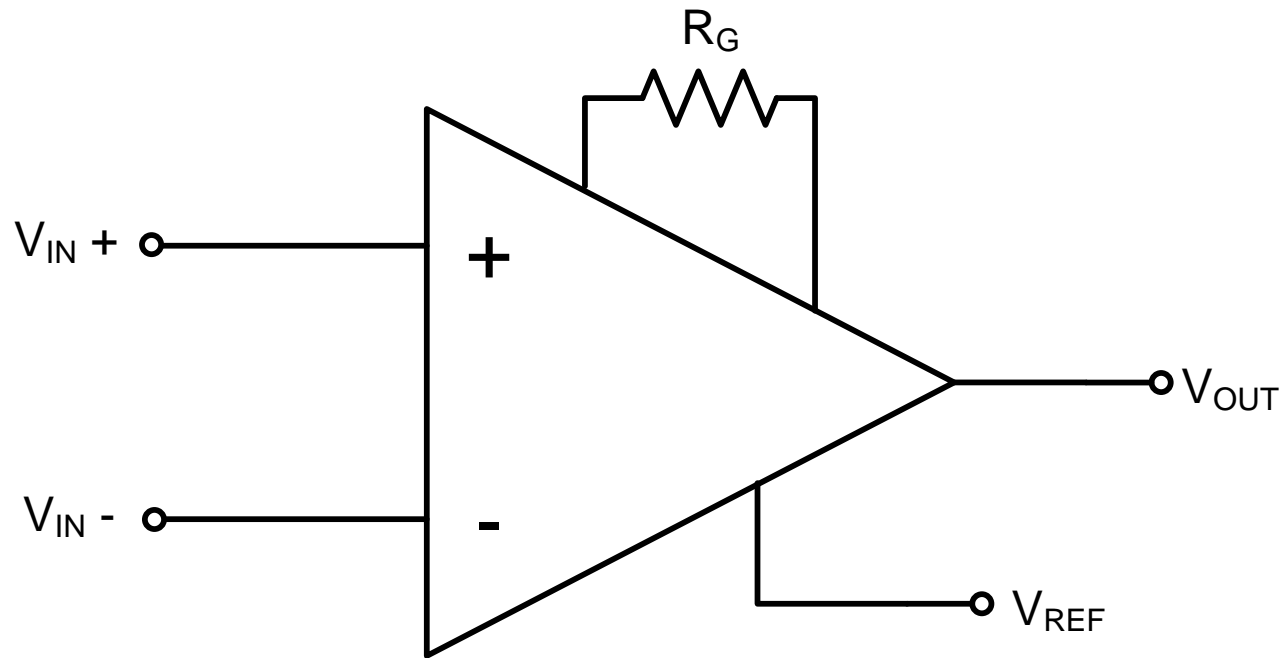

Three-Op-Amp In Amp

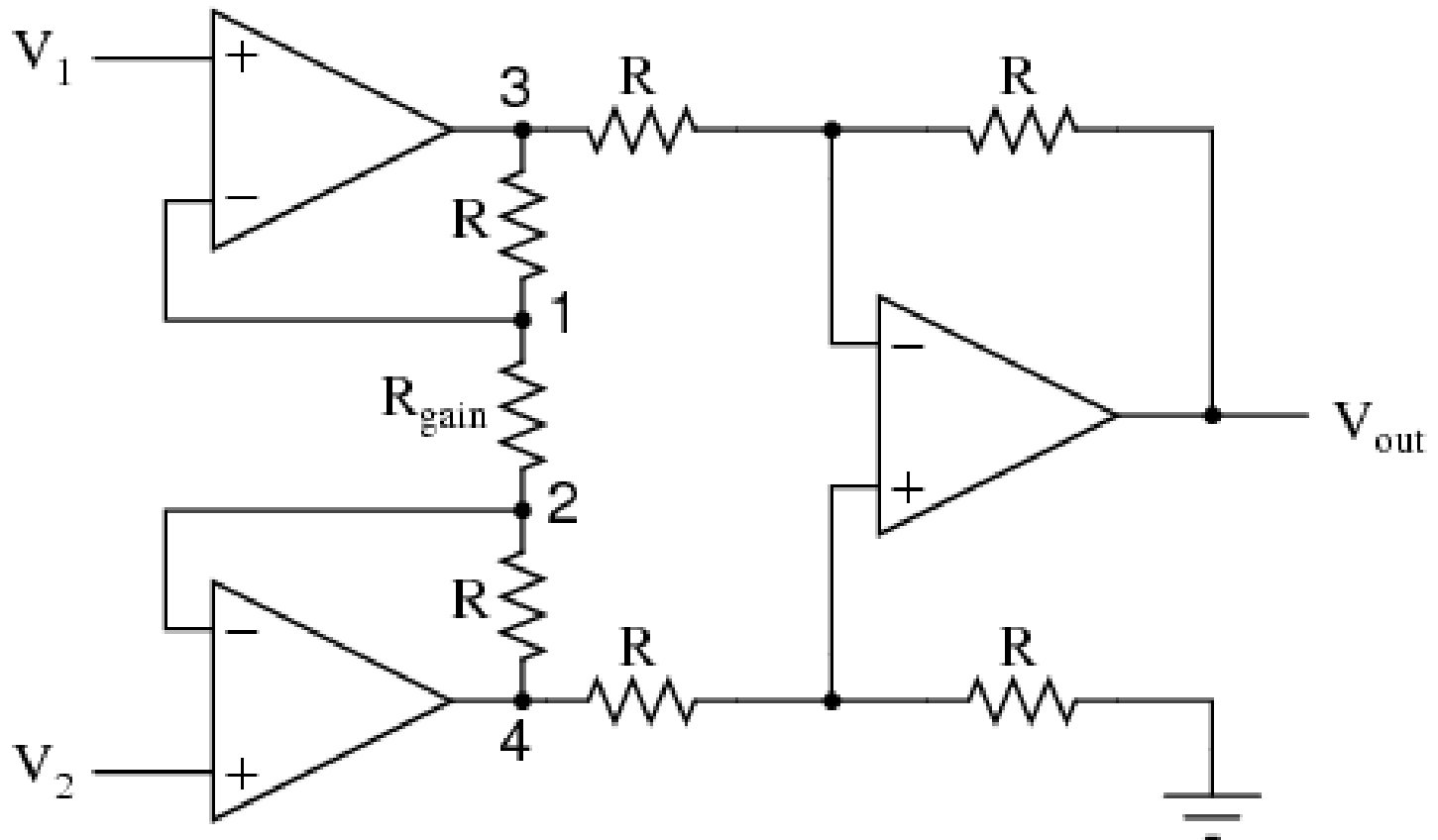

Two-Op-Amp In Amp

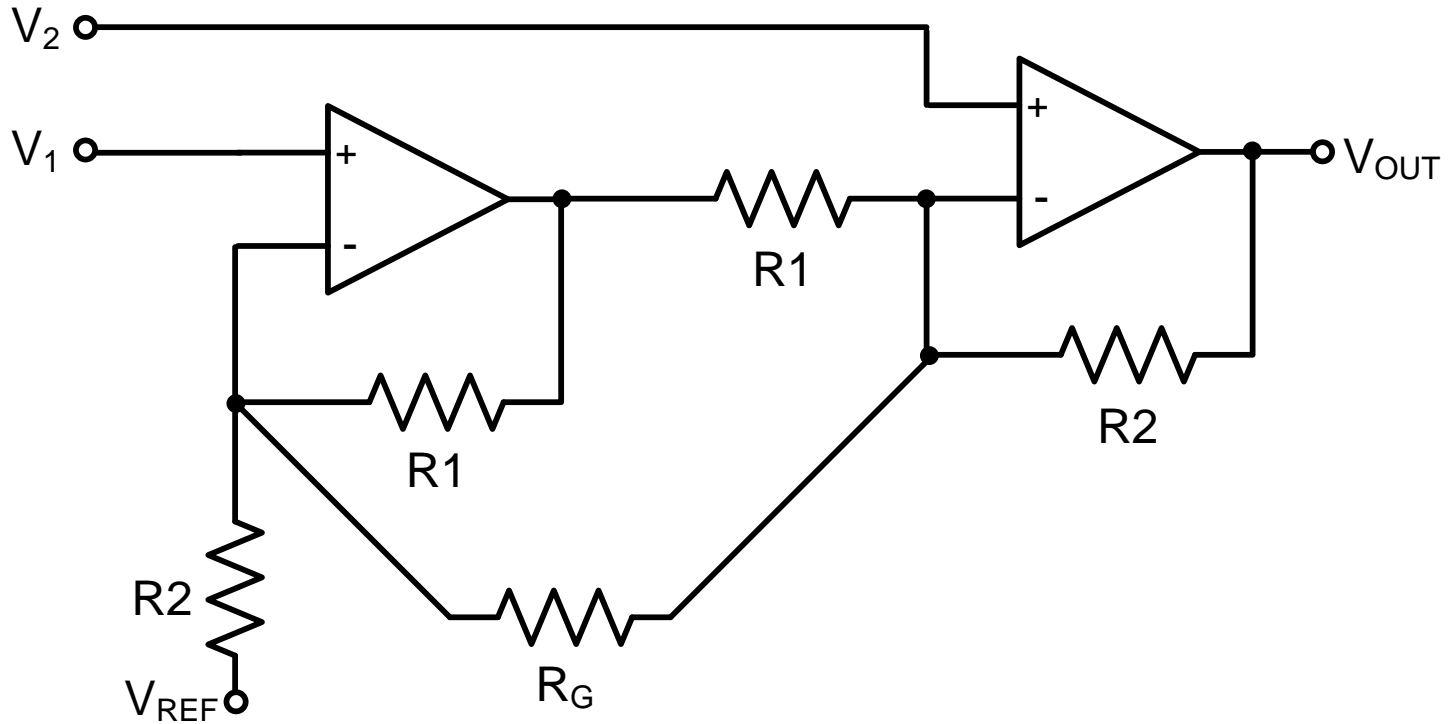

MCP602 - Single Supply Op Amp

Rail to Rail

Low Power

Cost \approx \$0.50



TSSOP



SOIC



PDIP

Vos Max	2000 μ V
Iq Typical	230 μ A
Iq Max	325 μ A
GBWP	2800 kHz
Operating Voltage Range	2.7 to 6.0 V
Input Voltage Noise Density	29 nV/rt(Hz)
PSRR Min	80 dB
CMRR Min	75 dB